

AN-31 Op Amp Circuit Collection

ABSTRACT

This application report provides basic circuits of the Texas Instruments op amp collection.

	Contents	
1	Introduction	
2	Basic Circuits	
3	Signal Generation	
4	Signal Processing	25
	List of Figures	
1	Inverting Amplifier	4
2	Non-Inverting Amplifier	4
3	Difference Amplifier	4
4	Inverting Summing Amplifier	5
5	Non-Inverting Summing Amplifier	5
6	Inverting Amplifier with High Input Impedance	5
7	Fast Inverting Amplifier with High Input Impedance	6
8	Non-Inverting AC Amplifier	6
9	Practical Differentiator	7
10	Integrator	7
11	Fast Integrator	8
12	Current to Voltage Converter	8
13	Circuit for Operating the LM101 Without a Negative Supply	ç
14	Circuit for Generating the Second Positive Voltage	ç
15	Neutralizing Input Capacitance to Optimize Response Time	ç
16	Integrator with Bias Current Compensation	10
17	Voltage Comparator for Driving DTL or TTL Integrated Circuits	10
18	Threshold Detector for Photodiodes	11
19	Double-Ended Limit Detector	11
20	Multiple Aperture Window Discriminator	12
21	Offset Voltage Adjustment for Inverting Amplifiers Using Any Type of Feedback Element	13
22	Offset Voltage Adjustment for Non-Inverting Amplifiers Using Any Type of Feedback Element	13
23	Offset Voltage Adjustment for Voltage Followers	13
24	Offset Voltage Adjustment for Differential Amplifiers	14
25	Offset Voltage Adjustment for Inverting Amplifiers Using 10 kΩ Source Resistance or Less	14
26	Low Frequency Sine Wave Generator with Quadrature Output	15
27	High Frequency Sine Wave Generator with Quadrature Output	16
28	Free-Running Multivibrator	16
29	-	17
30	-	17
All trademarks	s are the property of their respective owners.	





31	Pulse Width Modulator	18
32	Bilateral Current Source	18
33	Bilateral Current Source	19
34	Wein Bridge Oscillator with FET Amplitude Stabilization	20
35	Low Power Supply for Integrated Circuit Testing	21
36	Positive Voltage Reference	22
37	Positive Voltage Reference	22
38	Negative Voltage Reference	23
39	Negative Voltage Reference	23
40	Precision Current Sink	24
41	Precision Current Source	24
42	Differential-Input Instrumentation Amplifier	25
43	Variable Gain, Differential-Input Instrumentation Amplifier	26
44	Instrumentation Amplifier with ±100 Volt Common Mode Range	27
45	Instrumentation Amplifier with ±10 Volt Common Mode Range	28
46	High Input Impedance Instrumentation Amplifier	29
47	Bridge Amplifier with Low Noise Compensation	29
48	Bridge Amplifier	30
49	Precision Diode	30
50	Precision Clamp	31
51	Fast Half Wave Rectifier	31
52	Precision AC to DC Converter	32
53	Low Drift Peak Detector	32
54	Absolute Value Amplifier with Polarity Detector	33
55	Sample and Hold	
56	Sample and Hold	34
57	Low Drift Integrator	35
58	Fast [†] Summing Amplifier with Low Input Current	36
59	Fast Integrator with Low Input Current	37
60	Adjustable Q Notch Filter	38
61	Easily Tuned Notch Filter	39
62	Tuned Circuit	39
63	Two-Stage Tuned Circuit	40
64	Negative Capacitance Multiplier	40
65	Variable Capacitance Multiplier	41
66	Simulated Inductor	41
67	Capacitance Multiplier	42
68	High Pass Active Filter	42
69	Low Pass Active Filter	43
70	Nonlinear Operational Amplifier with Temperature Compensated Breakpoints	43
71	Current Monitor	44
72	Saturating Servo Preamplifier with Rate Feedback	44
73	Power Booster	45
74	Analog Multiplier	45
75	Long Interval Timer	46
76	Fast Zero Crossing Detector	46
77	Amplifier for Piezoelectric Transducer	47
78	Temperature Probe	47
79	Photodiode Amplifier	48



www.ti.com

80	Photodiode Amplifier	48
81	High Input Impedance AC Follower	48
82	Temperature Compensated Logarithmic Converter	49
83	Root Extractor	49
84	Multiplier/Divider	50
85	Cube Generator	50
86	Fast Log Generator	51
87	Anti-l og Generator	51



Introduction www.ti.com

1 Introduction

Texas Instruments recommends replacing 2N2920 and 2N3728 matched pairs with LM394 in all application circuits.

2 Basic Circuits

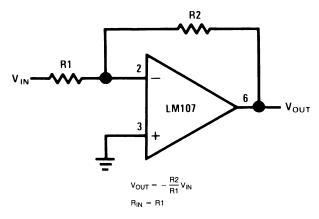


Figure 1. Inverting Amplifier


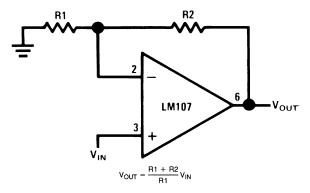


Figure 2. Non-Inverting Amplifier

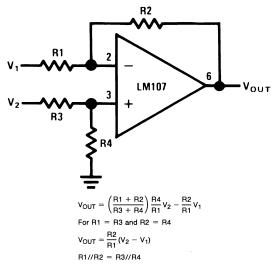


For minimum offset error due to input bias current.

Figure 3. Difference Amplifier




www.ti.com Basic Circuits

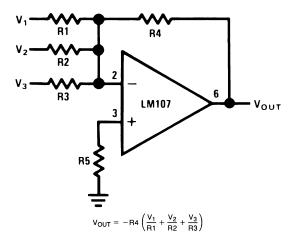

R5 = R1//R2//R3//R4


For minimum offset error due to input bias current/

Figure 4. Inverting Summing Amplifier

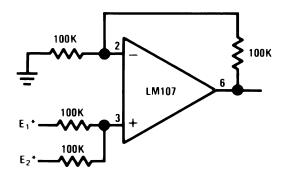

^{*} R_S = 1k for 1% accuracy

Figure 5. Non-Inverting Summing Amplifier

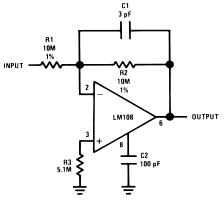

^{*} Source Impedance less than 100k gives less than 1% gain error.

Figure 6. Inverting Amplifier with High Input Impedance



Basic Circuits www.ti.com

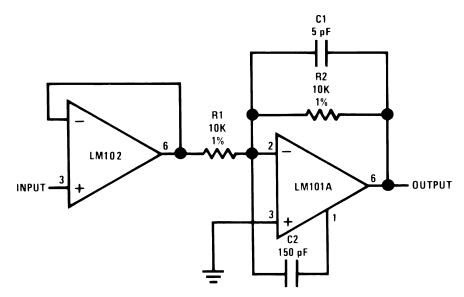


Figure 7. Fast Inverting Amplifier with High Input Impedance

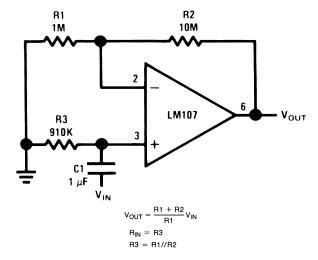


Figure 8. Non-Inverting AC Amplifier



www.ti.com Basic Circuits


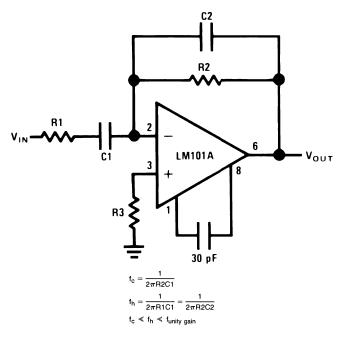


Figure 9. Practical Differentiator

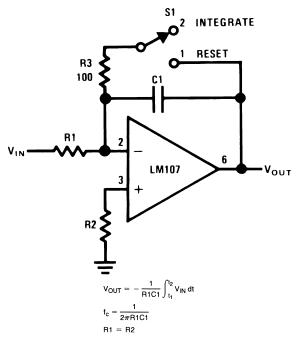

For minimum offset error due to input bias current.

Figure 10. Integrator



Basic Circuits www.ti.com


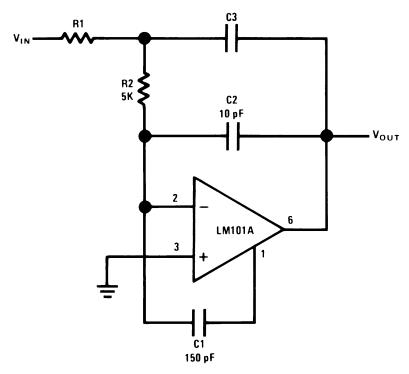


Figure 11. Fast Integrator

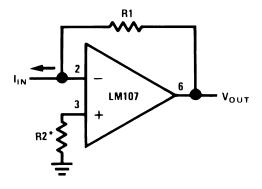

 $V_{\text{OUT}} = I_{\text{IN}} \; \text{R1}$ *For minimum error due to bias current R2 = R1

Figure 12. Current to Voltage Converter



www.ti.com Basic Circuits

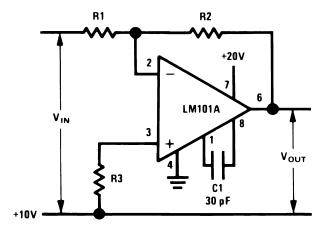


Figure 13. Circuit for Operating the LM101 Without a Negative Supply

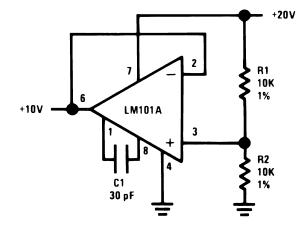


Figure 14. Circuit for Generating the Second Positive Voltage


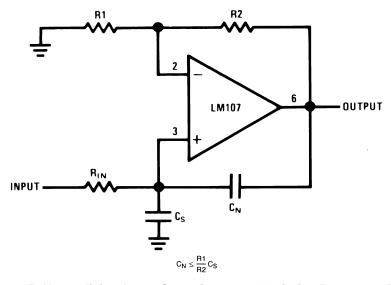


Figure 15. Neutralizing Input Capacitance to Optimize Response Time

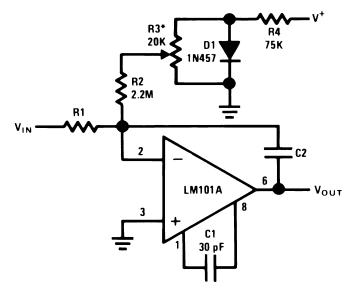

Basic Circuits www.ti.com



^{*} Adjust for zero integrator drift.

Current drift typically 0.1 n/A°C over −55°C to 125°C temperature range.

Figure 16. Integrator with Bias Current Compensation

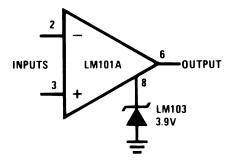


Figure 17. Voltage Comparator for Driving DTL or TTL Integrated Circuits



www.ti.com Basic Circuits


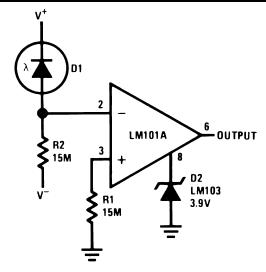


Figure 18. Threshold Detector for Photodiodes

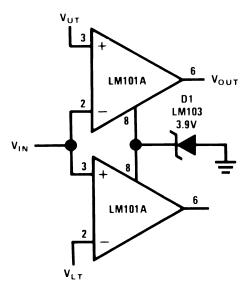

$$\begin{split} &V_{OUT} = 4.6 V \text{ for } V_{LT} \leq V_{IN} \leq V_{UT} \\ &V_{OUT} = 0 V \text{ for } V_{IN} < V_{LT} \text{ or } V_{IN} > V_{UT} \end{split}$$

Figure 19. Double-Ended Limit Detector



Basic Circuits www.ti.com

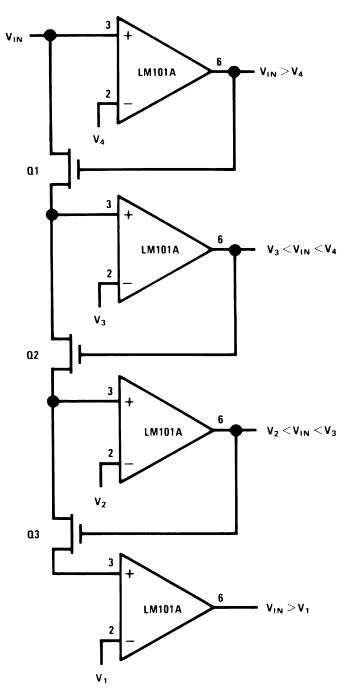


Figure 20. Multiple Aperture Window Discriminator



www.ti.com Basic Circuits

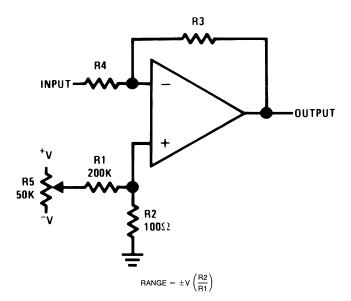


Figure 21. Offset Voltage Adjustment for Inverting Amplifiers Using Any Type of Feedback Element

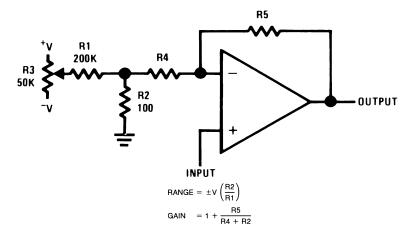


Figure 22. Offset Voltage Adjustment for Non-Inverting Amplifiers Using Any Type of Feedback Element

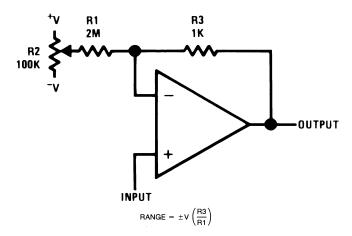


Figure 23. Offset Voltage Adjustment for Voltage Followers



Basic Circuits www.ti.com

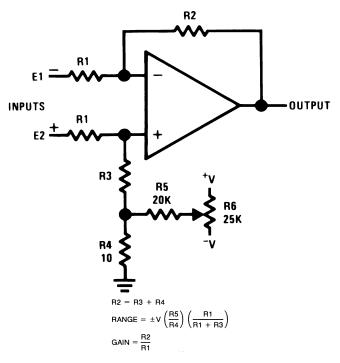


Figure 24. Offset Voltage Adjustment for Differential Amplifiers

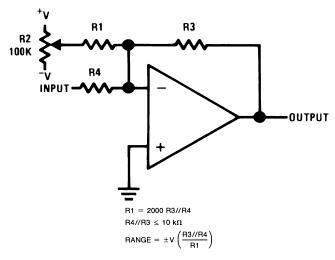


Figure 25. Offset Voltage Adjustment for Inverting Amplifiers Using 10 $k\Omega$ Source Resistance or Less



www.ti.com Signal Generation

3 Signal Generation

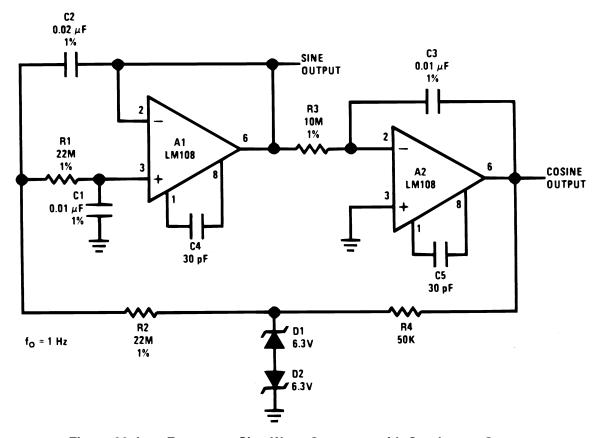


Figure 26. Low Frequency Sine Wave Generator with Quadrature Output



Signal Generation www.ti.com


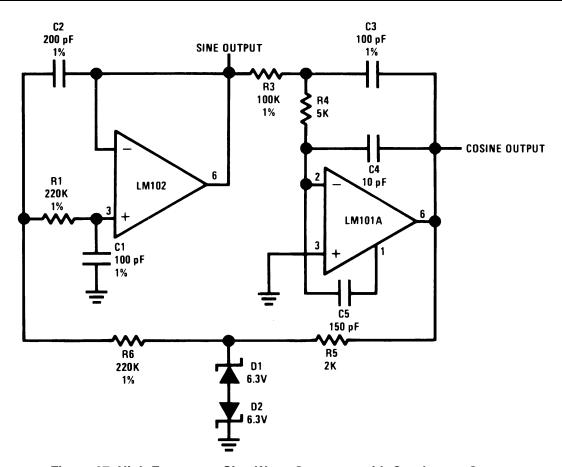


Figure 27. High Frequency Sine Wave Generator with Quadrature Output

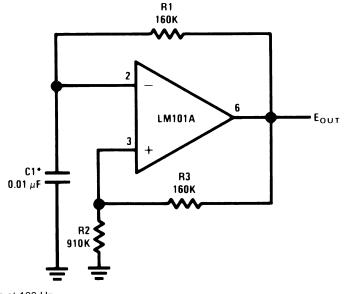


* Chosen for oscillation at 100 Hz

Figure 28. Free-Running Multivibrator



www.ti.com Signal Generation

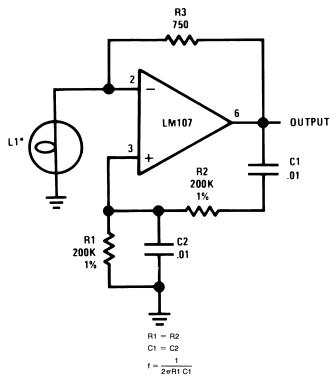

^{*} Eldema 1869 10V, 14 mA Bulb

Figure 29. Wein Bridge Sine Wave Oscillator

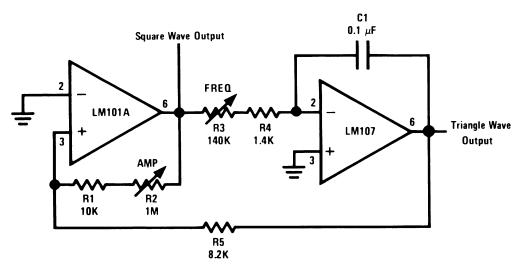


Figure 30. Function Generator



Signal Generation www.ti.com

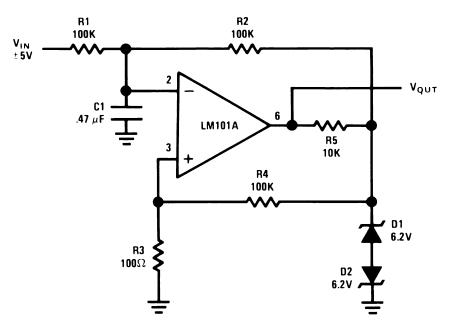


Figure 31. Pulse Width Modulator

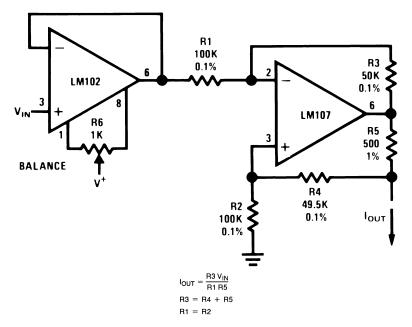


Figure 32. Bilateral Current Source



www.ti.com Signal Generation

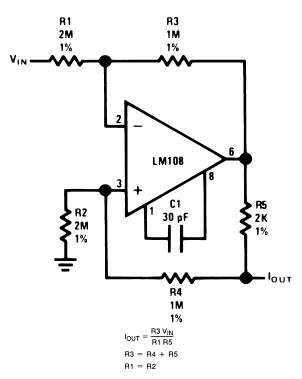


Figure 33. Bilateral Current Source



Signal Generation www.ti.com


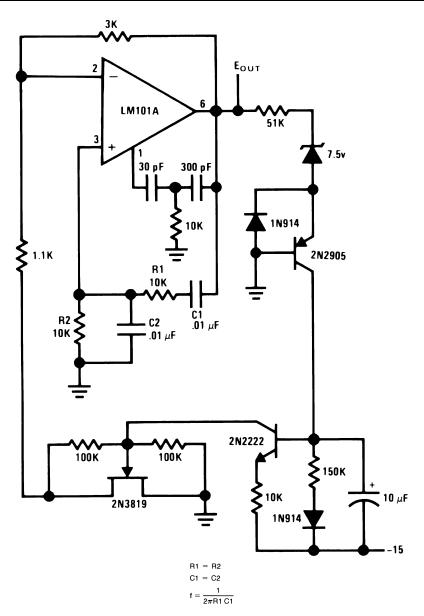


Figure 34. Wein Bridge Oscillator with FET Amplitude Stabilization

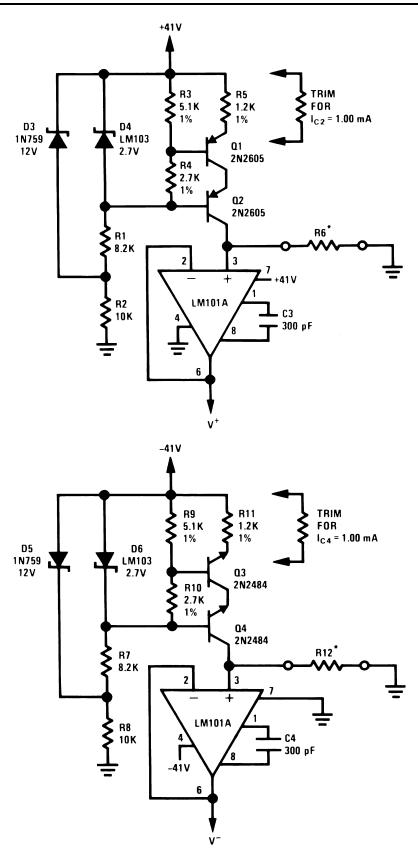

www.ti.com Signal Generation



^{*} $V_{OUT} = 1V/k\Omega$

Figure 35. Low Power Supply for Integrated Circuit Testing



Signal Generation www.ti.com

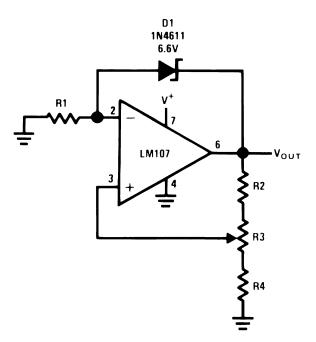


Figure 36. Positive Voltage Reference

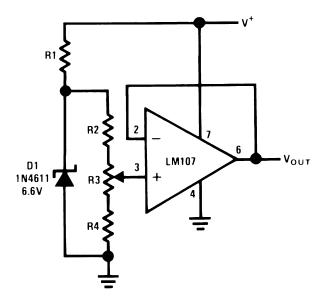


Figure 37. Positive Voltage Reference



www.ti.com Signal Generation

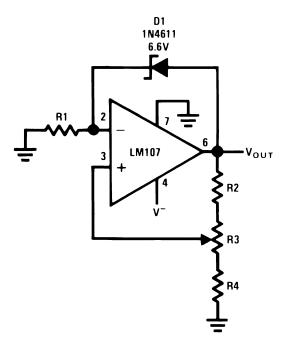


Figure 38. Negative Voltage Reference

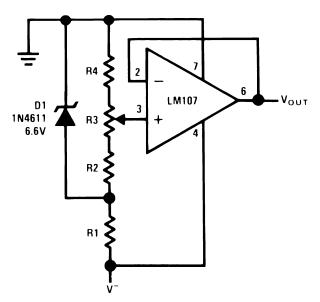


Figure 39. Negative Voltage Reference



Signal Generation www.ti.com

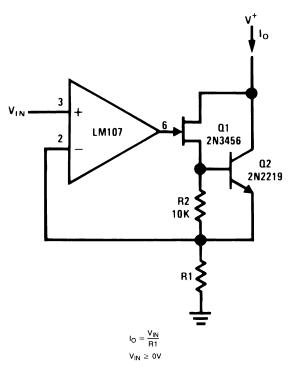


Figure 40. Precision Current Sink

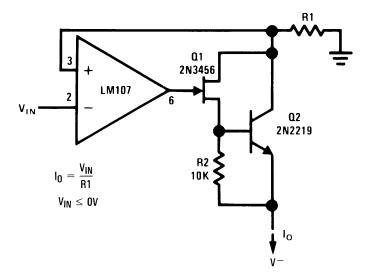


Figure 41. Precision Current Source



www.ti.com Signal Processing

4 Signal Processing


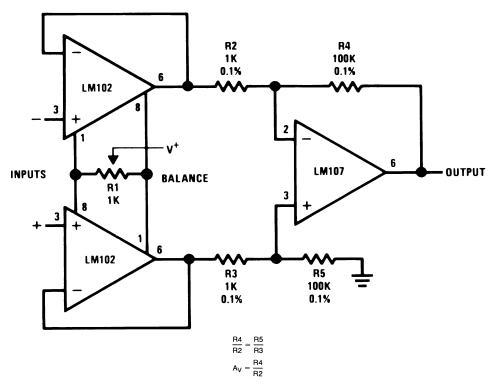


Figure 42. Differential-Input Instrumentation Amplifier

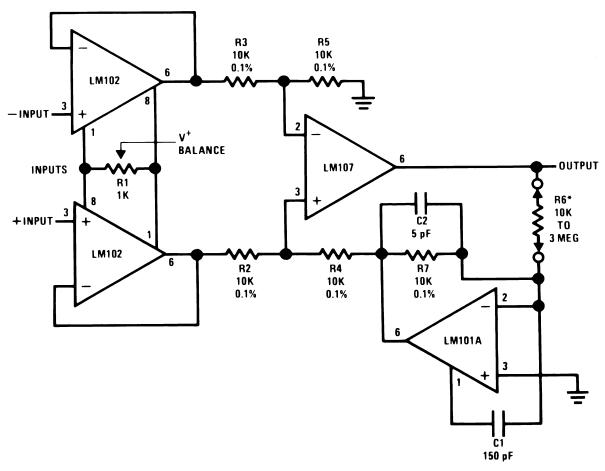

Signal Processing www.ti.com




^{*} Gain adjust $A_V = 10^{-4} R6$

Figure 43. Variable Gain, Differential-Input Instrumentation Amplifier



www.ti.com Signal Processing

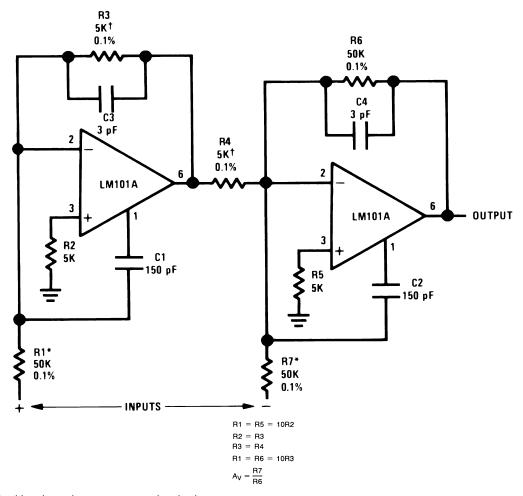

† Matching determines common mode rejection.

Figure 44. Instrumentation Amplifier with ±100 Volt Common Mode Range



Signal Processing www.ti.com


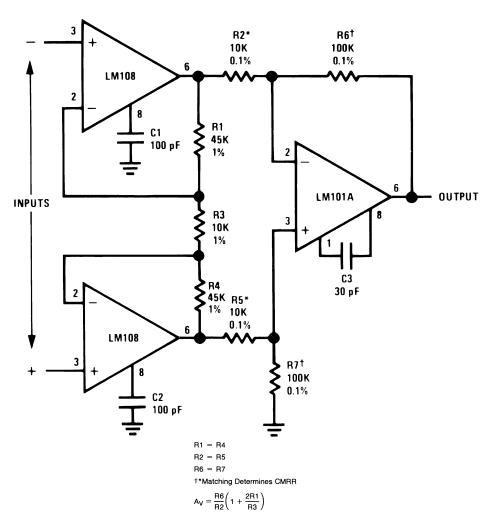


Figure 45. Instrumentation Amplifier with ±10 Volt Common Mode Range

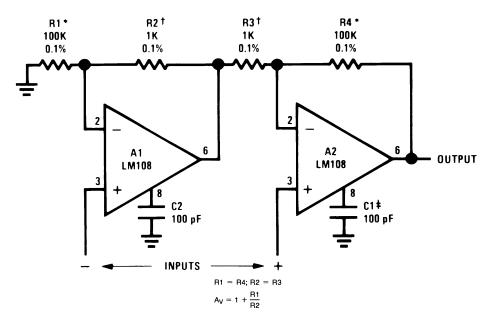


www.ti.com Signal Processing



^{*†} Matching Determines CMRR

Figure 46. High Input Impedance Instrumentation Amplifier

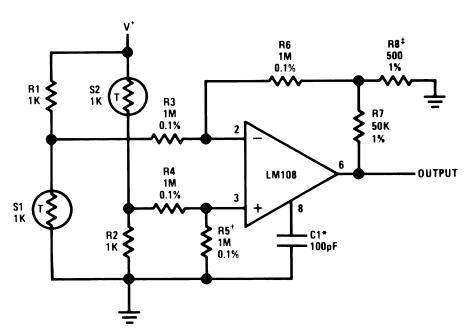

^{*} Reduces feed through of power supply noise by 20 dB and makes supply bypassing unnecessary.

Figure 47. Bridge Amplifier with Low Noise Compensation

[‡] May be deleted to maximize bandwidth

[†] Trim for best common mode rejection

[‡] Gain adjust



Signal Processing www.ti.com

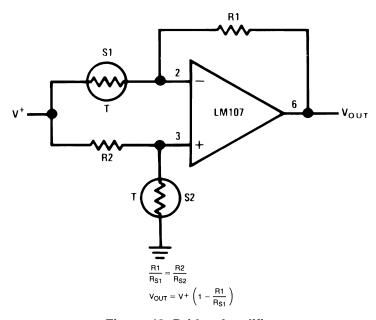


Figure 48. Bridge Amplifier


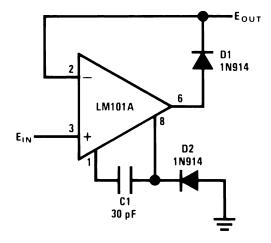


Figure 49. Precision Diode

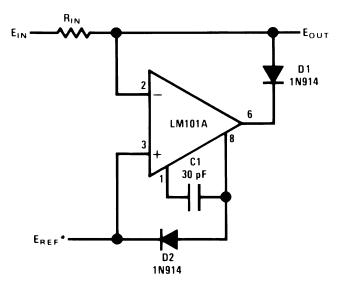

Signal Processing www.ti.com



 $^{^{\}star}$ E_{REF} must have a source impedance of less than 200Ω if D2 is used.

Figure 50. Precision Clamp


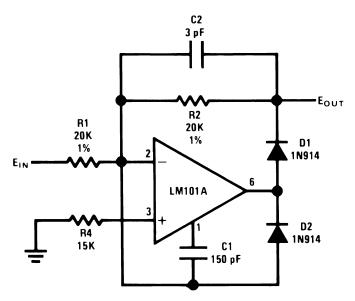


Figure 51. Fast Half Wave Rectifier

31

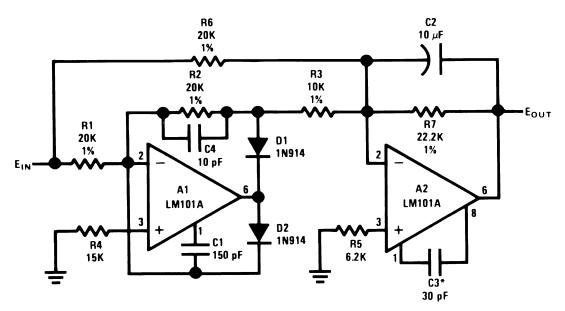

Signal Processing www.ti.com



^{*} Feedforward compensation can be used to make a fast full wave rectifier without a filter.

Figure 52. Precision AC to DC Converter

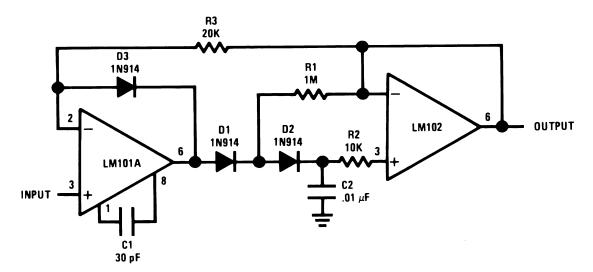


Figure 53. Low Drift Peak Detector



www.ti.com Signal Processing


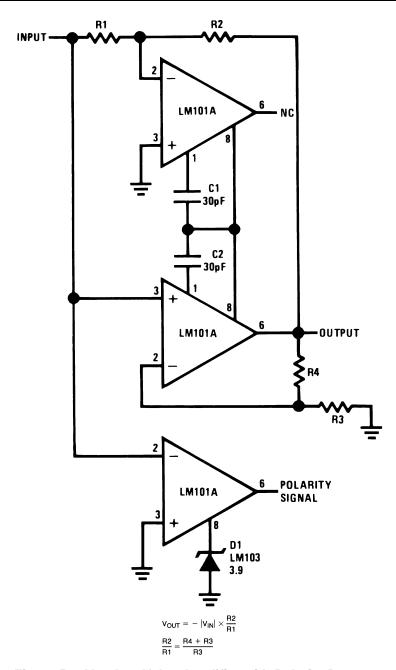


Figure 54. Absolute Value Amplifier with Polarity Detector

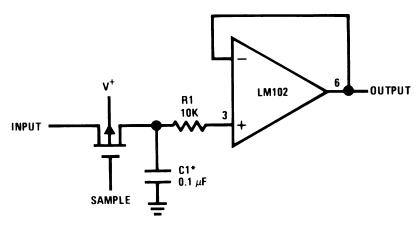


Signal Processing www.ti.com



^{*} Polycarbonate-dielectric capacitor

Figure 55. Sample and Hold

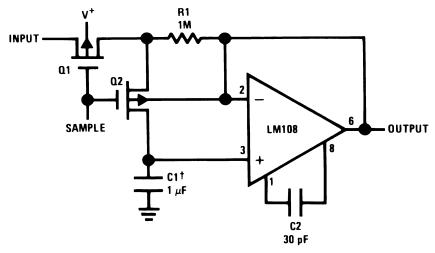


^{*} Worst case drift less than 2.5 mV/sec

Figure 56. Sample and Hold

[†] Teflon, Polyethylene or Polycarbonate Dielectric Capacitor



www.ti.com Signal Processing

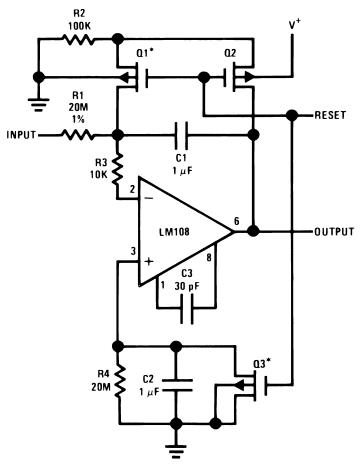


^{*} Q1 and Q3 should not have internal gate-protection diodes. Worst case drift less than 500 μ V/sec over -55°C to +125°C.

Figure 57. Low Drift Integrator



Signal Processing www.ti.com

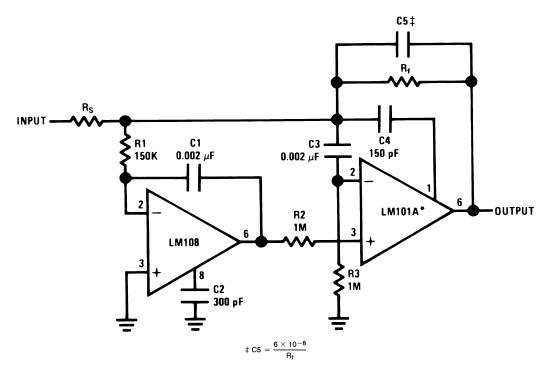

^{*} In addition to increasing speed, the LM101A raises high and low frequency gain, increases output drive capability and eliminates thermal feedback.

† Power Bandwidth: 250 kHz Small Signal Bandwidth: 3.5 MHz

Slew Rate: 10V/µs

Figure 58. Fast† Summing Amplifier with Low Input Current



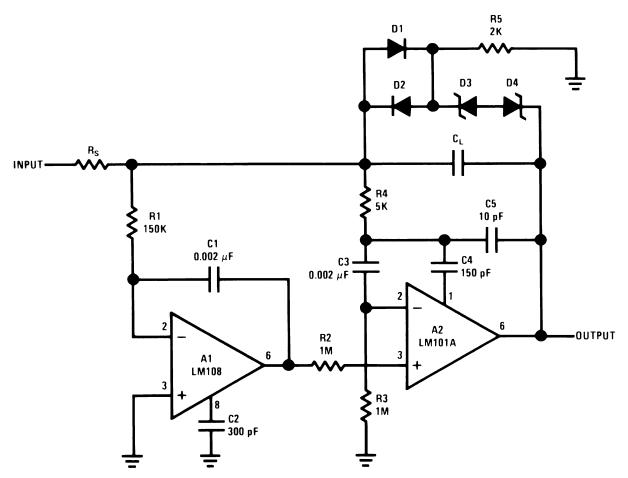


Figure 59. Fast Integrator with Low Input Current



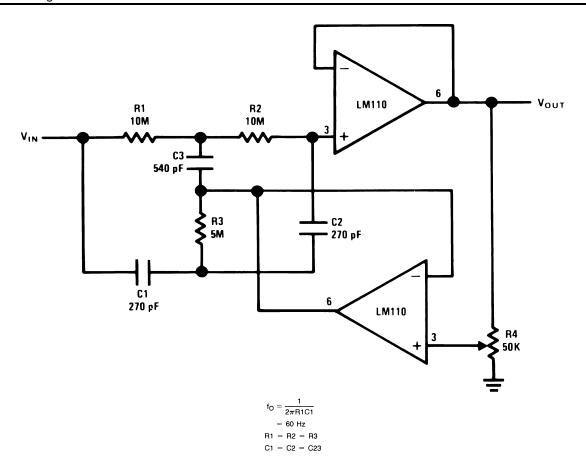


Figure 60. Adjustable Q Notch Filter



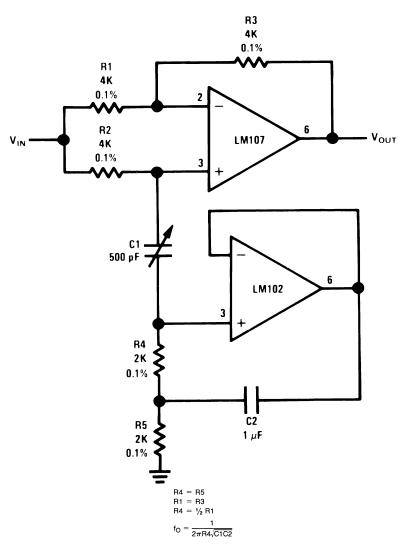


Figure 61. Easily Tuned Notch Filter

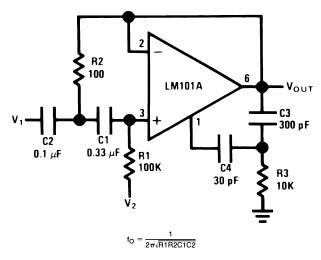


Figure 62. Tuned Circuit



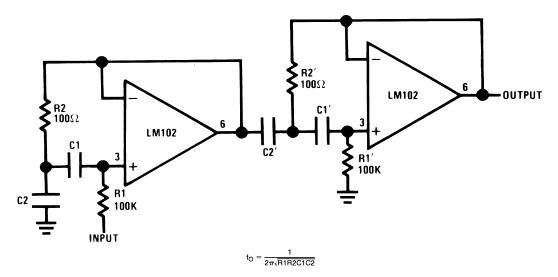


Figure 63. Two-Stage Tuned Circuit

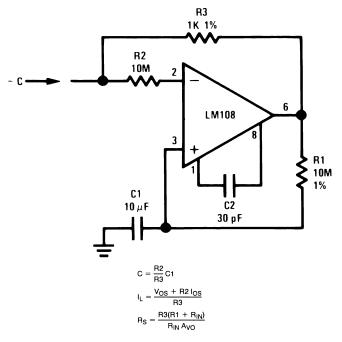


Figure 64. Negative Capacitance Multiplier




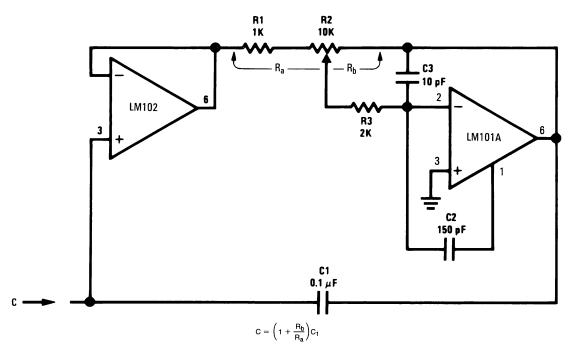


Figure 65. Variable Capacitance Multiplier

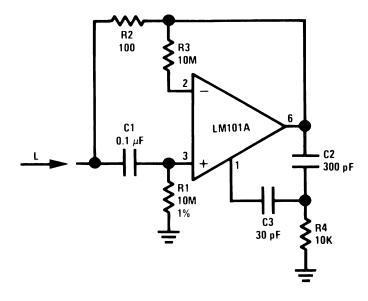

 $L \ge R1 R2 C1$ $R_S = R2$ $R_P = R1$

Figure 66. Simulated Inductor




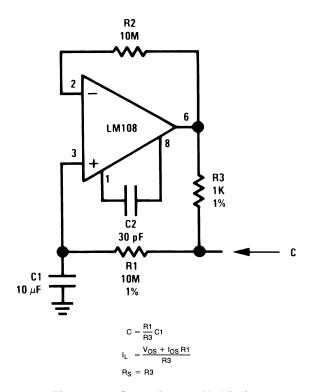



Figure 67. Capacitance Multiplier

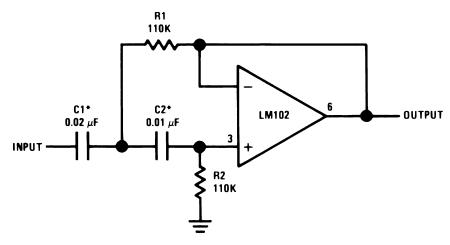

^{*} Values are for 100 Hz cutoff. Use metalized polycarbonate capacitors for good temperature stability.

Figure 68. High Pass Active Filter



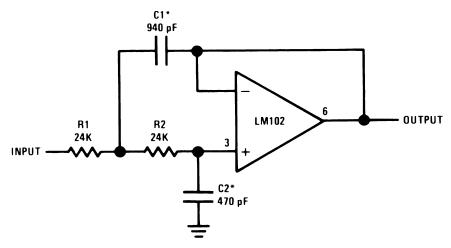

^{*} Values are for 10 kHz cutoff. Use silvered mica capacitors for good temperature stability.

Figure 69. Low Pass Active Filter

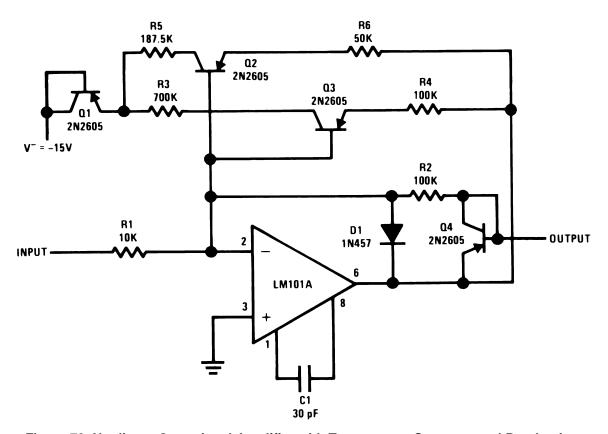


Figure 70. Nonlinear Operational Amplifier with Temperature Compensated Breakpoints



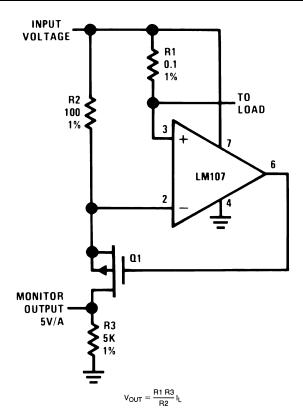


Figure 71. Current Monitor

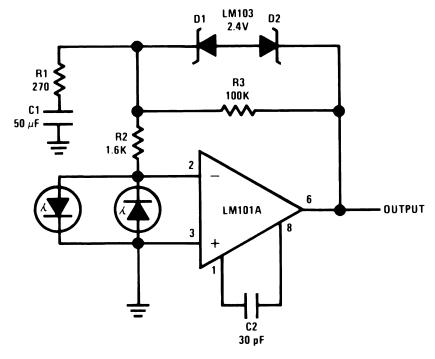


Figure 72. Saturating Servo Preamplifier with Rate Feedback



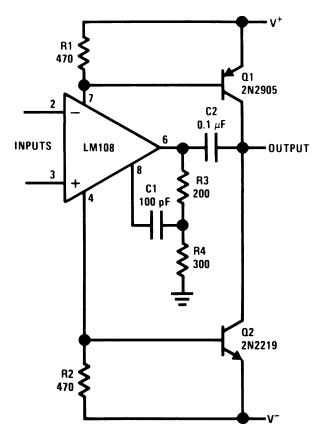


Figure 73. Power Booster


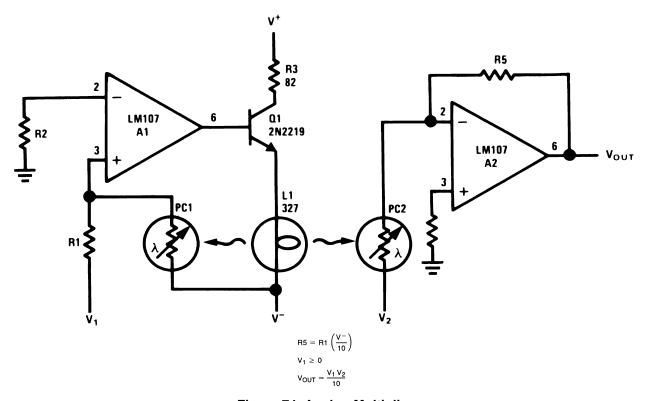



Figure 74. Analog Multiplier

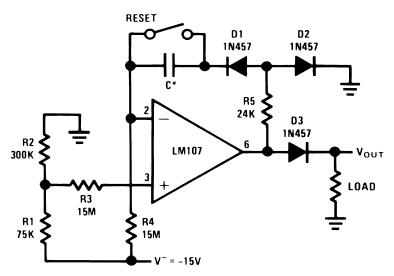



^{*} Low leakage -0.017 µF per second delay


Figure 75. Long Interval Timer

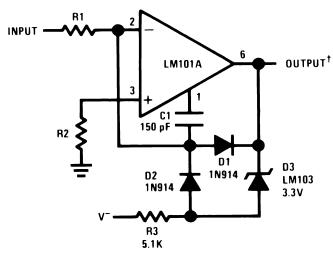

Propagation delay approximately 200 ns † DTL or TTL fanout of three. Minimize stray capacitance Pin 8


Figure 76. Fast Zero Crossing Detector



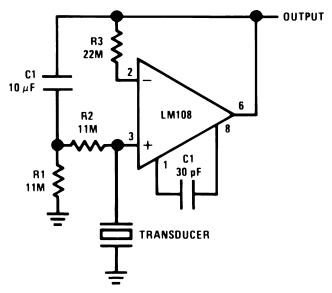

Low frequency cutoff = R1 C1


Figure 77. Amplifier for Piezoelectric Transducer

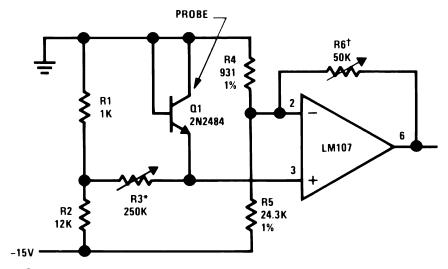

- * Set for 0V at 0°C
- † Adjust for 100 mV/°C


Figure 78. Temperature Probe



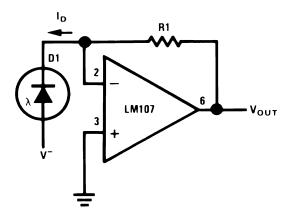

 $V_{OUT} = R1 I_D$

Figure 79. Photodiode Amplifier

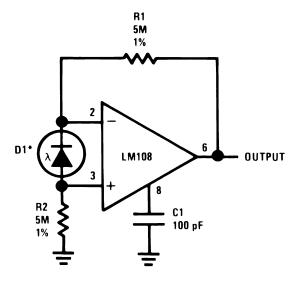

 $V_{OUT} = 10 \text{ V/}\mu\text{A}$

Figure 80. Photodiode Amplifier


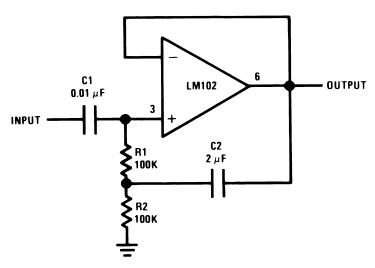


Figure 81. High Input Impedance AC Follower

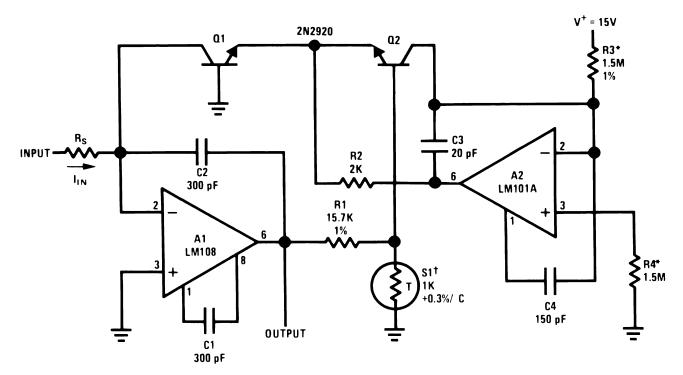^{*}Operating photodiode with less than 3 mV across it eliminates leakage currents.





10 nA < $I_{\rm IN}$ < 1 mA Sensitivity is 1V per decade

† 1 k Ω (±1%) at 25°C, +3500 ppm/°C.

Available from Vishay Ultronix, Grand Junction, CO, Q81 Series.

Figure 82. Temperature Compensated Logarithmic Converter

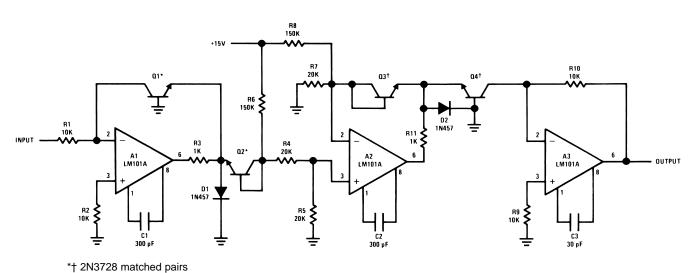


Figure 83. Root Extractor

 $^{^{\}star}$ Determines current for zero crossing on output: 10 μA as shown.



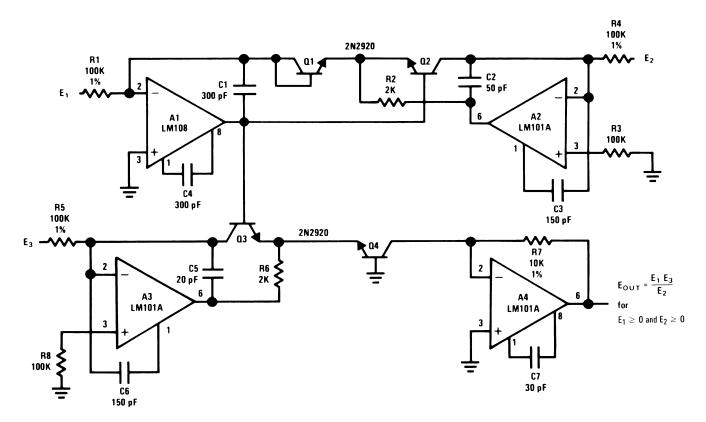


Figure 84. Multiplier/Divider


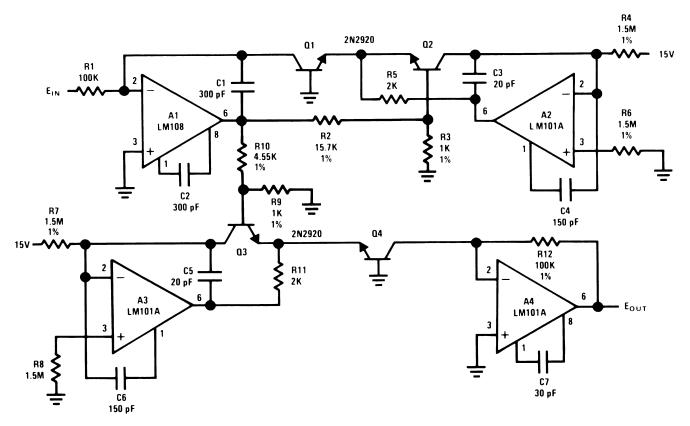



Figure 85. Cube Generator

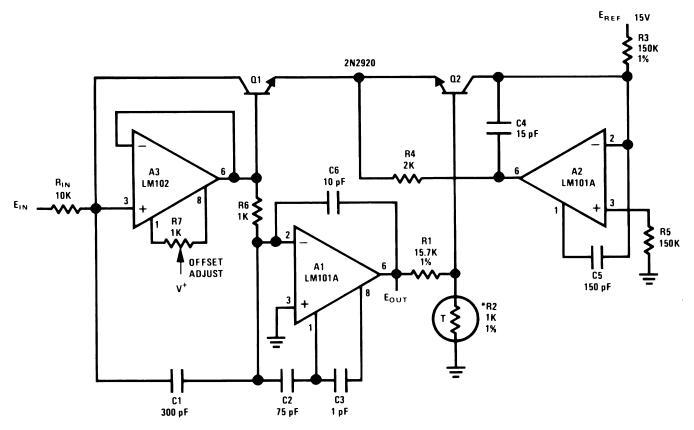



† 1 k Ω (±1%) at 25°C, +3500 ppm/°C. Available from Vishay Ultronix, Grand Junction, CO, Q81 Series.

Figure 86. Fast Log Generator

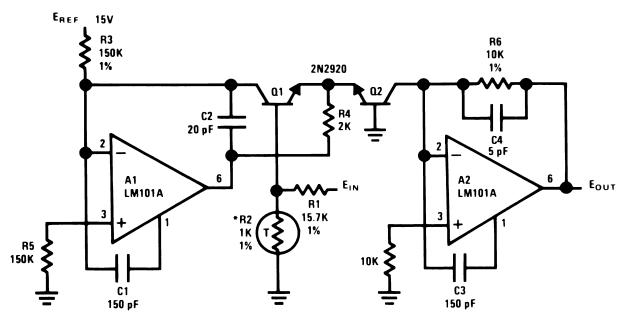

† 1 k Ω (±1%) at 25°C, +3500 ppm/°C. Available from Vishay Ultronix, Grand Junction, CO, Q81 Series.

Figure 87. Anti-Log Generator

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products Applications

Audio www.ti.com/audio Automotive and Transportation www.ti.com/automotive Communications and Telecom **Amplifiers** amplifier.ti.com www.ti.com/communications **Data Converters** dataconverter.ti.com Computers and Peripherals www.ti.com/computers **DLP® Products** www.dlp.com Consumer Electronics www.ti.com/consumer-apps

DSP **Energy and Lighting** dsp.ti.com www.ti.com/energy Clocks and Timers www.ti.com/clocks Industrial www.ti.com/industrial Interface interface.ti.com Medical www.ti.com/medical logic.ti.com Logic Security www.ti.com/security

Power Mgmt power.ti.com Space, Avionics and Defense www.ti.com/space-avionics-defense

Microcontrollers <u>microcontroller.ti.com</u> Video and Imaging <u>www.ti.com/video</u>

RFID www.ti-rfid.com

OMAP Applications Processors www.ti.com/omap TI E2E Community e2e.ti.com

Wireless Connectivity <u>www.ti.com/wirelessconnectivity</u>